


Filter Design Report

Design: Lowpass Filter - 2nd order Butterworth

Design ID: 32

Type : Lowpass Response : Butterworth Order : 2

Number of Stages: 1

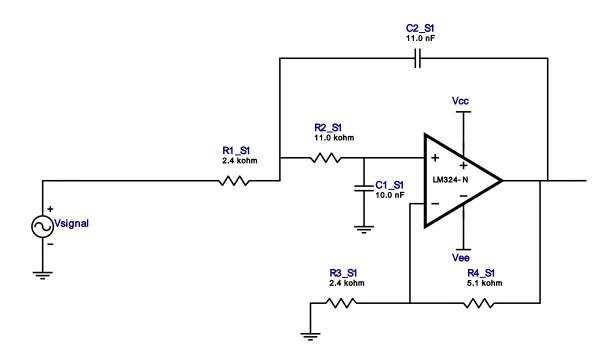


#### **Electrical BOM**

#	Name	Manufacturer	Part Number	Properties	Qty
1.	A1_S1	Texas Instruments Inc.	LM324-N	GbwTyp= 1MHz VccMax= 32V VccMin= 3V	1
2.	C1_S1	Generic	Ideal	Cap= 10.0 nF Tolerance= 2.0 %	1
3.	C2_S1	Generic	Ideal	Cap= 11.0 nF Tolerance= 2.0 %	1
4.	R1_S1	Generic	Ideal	Res= 2400.0ohm Tolerance= 1%	1
5.	R2_S1	Generic	Ideal	Res= 11000.0ohm Tolerance= 1%	1
6.	R3_S1	Generic	Ideal	Res= 2400.0ohm Tolerance= 1%	1
7.	R4_S1	Generic	Ideal	Res= 5100.0ohm Tolerance= 1%	1

# Sensitivity Analysis

#	Name	Series	Tolerance
1.	Сар	E48	2%
2.	Res	E96	1%

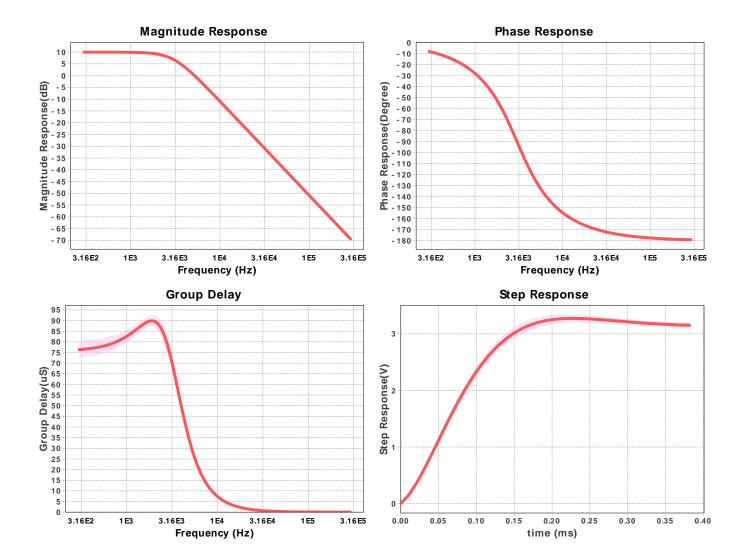

# **Design Inputs**


#	Name	Value	Description
1.	FilterType	lowpass	·
2.	FilterResponse	Butterworth	
3.	FilterOrder	2.0	
4.	FilterTopology	Sallen-Key	
5.	NumberOfStages	1.0	
6.	PassbandFrequency	3.0 k	
7.	StopbandAttenuation	-40.001	
8.	StopbandFrequency	30.0 k	
9.	Gain	3.162	
10.	DualSupply	+/-5.00 V	Power supply(s) to active chips
11.	ResistorTolerance	E96	Resistor series - 1% Passive resistor tolerance
12.	CapacitorTolerance	E48	Capacitor series - 2% Passive capacitor tolerance

# Design Assistance

 $1. \ \textbf{LM324-N} \ Product \ Folder: http://www.ti.com/product/LM324-N: contains \ the \ data \ sheet \ and \ other \ resources.$ 
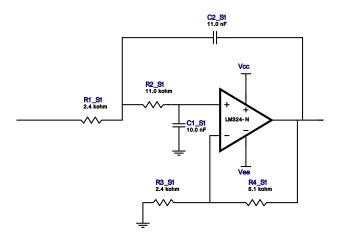
# Filter Stage :1

Cutoff Frequency2.953 kHzMin GBW Reqd670.814 kHzStage Gain3.125 V/VStage Q691.769 mStage TopologySallen-Key



#### **Electrical BOM**

#	Name	Manufacturer	Part Number	Properties	Qty
1.	A1_S1	Texas Instruments Inc.	LM324-N	GbwTyp= 1MHz VccMax= 32V VccMin= 3V	1
2.	C1_S1	Generic	Ideal	Cap= 10.0 nF Tolerance= 2.0 %	1
3.	C2_S1	Generic	Ideal	Cap= 11.0 nF Tolerance= 2.0 %	1
4.	R1_S1	Generic	Ideal	Res= 2400.0ohm Tolerance= 1%	1
5.	R2_S1	Generic	Ideal	Res= 11000.0ohm Tolerance= 1%	1
6.	R3_S1	Generic	Ideal	Res= 2400.0ohm Tolerance= 1%	1

#	Name	Manufacturer	Part Number	Properties	Qty
7.	R4_S1	Generic	Ideal	Res= 5100.0ohm Tolerance= 1%	1

#### Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.